

PHYS 241 Assignment 2.

Mihail Anghelici 260928404

Question1.

a)

The relative permittivity ϵ_r is a textbook value given by 2.1. The vacuum permittivity value is approximately $8.85 \times 10^{-12} \text{ F m}^{-1}$. The capacitance C is then given by

$$\begin{aligned} C &= \frac{\epsilon_0 \epsilon_r A}{d} \\ &= \frac{(0.01)^2 (2.1) (8.85 \times 10^{-12})}{0.0001} \left[\frac{\text{m}^2 \text{ F}}{\text{m}^2} \right] \\ &= 1.8585 \times 10^{-11} \text{ F} = \boxed{18.585 \text{ pF}}. \end{aligned}$$

b)

The circuit time constant for an RC set up is given by

$$\begin{aligned} \tau = RC &= (1 \times 10^3) (1.8585 \times 10^{-11}) \Omega \text{ F} \\ &= 1.8585 \times 10^{-8} \text{ s} = \boxed{0.018585 \mu\text{s}}. \end{aligned}$$

c)

The formula for a capacitor's charge who's discharging is given by

$$\begin{aligned} Q(t) &= Q_{\max} \left(1 - e^{\frac{-t}{\tau}} \right) \\ 5 \text{ C} &= 10 \text{ C} (1 - e^{\frac{-t}{0.018585 \text{ s}}}) \\ (-0.01858 \text{ s}) \left(\ln \left(\frac{1 \text{ s}}{2 \text{ s}} \right) \right) &\implies \boxed{t = 0.01288 \text{ s}}. \end{aligned}$$

d)

The total energy dissipated across a resistor from a capacitor is given by

$$\begin{aligned} U_C(t) &= \frac{1}{2} C (\Delta V_C(t))^2 \\ &= \frac{1}{2} C \left(\frac{Q}{C} \right)^2 \\ &= \frac{1}{2} \frac{Q^2}{C} \\ \Rightarrow U_C(0.01288 \text{ s}) &= \frac{1}{2} \frac{(5 \times 10^{-6})^2}{(1.8585 \times 10^{-11})} \left[\frac{\text{C}^2}{\text{F}} \right] \\ &= \boxed{0.6726 \text{ J}}. \end{aligned}$$

Question 2.

a)

The inductance is given by

$$\begin{aligned} L = \mu_0 A \frac{N^2}{\ell} &= 4\pi \times 10^{-7} (0.01)^2 \pi \frac{(1000)^2}{0.05} \left[\frac{\text{H m}^2}{\text{m}^2} \right] \\ &= 7.895 \times 10^{-3} \text{ H} = \boxed{7.895 \text{ mH}}. \end{aligned}$$

b)

The time constant for a LR circuit is given by

$$\tau = \frac{L}{R} = \frac{7.895 \times 10^{-3} \text{ H}}{1 \times 10^3 \Omega} = 7.895 \text{ s} = \boxed{7.896 \times 10^6 \mu\text{s}}.$$

c)

The maximal value for the current in the given circuit is $I_{\max} = \frac{V_0}{R}$. Thus the time to reach the half value of I_{\max} is

$$\begin{aligned}\frac{I_{\max}}{2} &= I_{\max} \left(e^{\frac{-t_{1/2}}{\tau}} \right) \\ \ln \left(\frac{1}{2} \right) (-\tau) &= t_{1/2} \\ \Rightarrow t_{1/2} &= \ln \left(\frac{1}{2} \right) (-7.896) = \boxed{5.472 \text{ s}}.\end{aligned}$$

Question 3.

Let $R_{\text{eq}} = R_1 + R_2$ since the two resistors are in series.

a)

$$V_0 = \Delta V_C + \Delta V_{R_{\text{eq}}} = \frac{Q}{C} + IR_{\text{eq}}$$

Let us apply a time derivative on both sides , since $I = I(t)$ and $Q = Q(t)$ this yields ,

$$0 = \frac{1}{C} \frac{dQ}{dt} + R_{\text{eq}} \frac{dI}{dt}.$$

Since $\frac{dQ}{dt} = I$, we have

$$\begin{aligned}\frac{dI}{dt} &= \frac{-I}{CR_{\text{eq}}} \\ \Rightarrow \frac{dI}{dt} + \frac{I}{\tau} &= 0 \quad \text{for } \tau = C(R_1 + R_2).\end{aligned}$$

b)

At $t = 0$, the capacitor is fully discharged, so only the resistor plays a role such that

$$I_0 = \frac{V_0}{R_{\text{eq}}}.$$

c)

Note that $\frac{dI}{dt} = \frac{-I}{CR_{\text{eq}}}$ is a separable equation. Therefore ,

$$\begin{aligned}\frac{dI}{dt} = \frac{-I}{CR_{\text{eq}}} &\implies CR_{\text{eq}} \frac{I'}{I} = -1 \implies CR_{\text{eq}} \ln(I) = \int -1 dt \\ &\implies CR_{\text{eq}} \ln(I) = -t + c \implies I - e^{\frac{-t+c}{CR_{\text{eq}}}} = e^{\frac{-t}{CR_{\text{eq}}}} e^{\frac{c}{CR_{\text{eq}}}}.\end{aligned}$$

Define $A = e^{\frac{c}{CR_{\text{eq}}}}$ then we have the initial value problem

$$\begin{aligned}I &= Ae^{\frac{-t}{CR_{\text{eq}}}}, I(0) = \frac{V_0}{R_{\text{eq}}} \\ \frac{V_0}{R_{\text{eq}}} &= Ae^{\frac{0}{CR_{\text{eq}}}} \implies A = \frac{V_0}{R_{\text{eq}}}\end{aligned}$$

thus the desired differential equation is $I(t) = \frac{V_0}{R_{\text{eq}}} e^{\frac{-t}{\tau}}$ for $\tau = C(R_1 + R_2)$.

d)

Since $I(t) = \frac{V_0}{R_{\text{eq}}} e^{\frac{-t}{\tau}}$, then $IR = V_0 e^{\frac{-t}{\tau}}$. Using conservation of voltage along the circuit along with the substitution for IR we have

$$\begin{aligned}\Delta V_C(t) &= \frac{1}{C} Q(t) = V_0 - IR = V_0 - V_0 e^{\frac{-t}{\tau}} = V_0(1 - e^{\frac{-t}{\tau}}) \\ \text{Since } Q &= C\Delta V_C, \text{ we have } C\Delta V_C = CV_0(1 - e^{\frac{-t}{\tau}}) \\ &\implies Q(t) = CV_0(1 - e^{\frac{-t}{\tau}}).\end{aligned}$$

e)

Since $\Delta V_C = V_0(1 - e^{\frac{-t}{\tau}})$, then since the capacitor is charging and voltage drop is conserved throughout the circuit, symmetrically , we have

$$\Delta V_{R_2}(t) = \left(\frac{R_2}{R_1 + R_2} \right) V_0 e^{\frac{-t}{\tau}}$$

f)

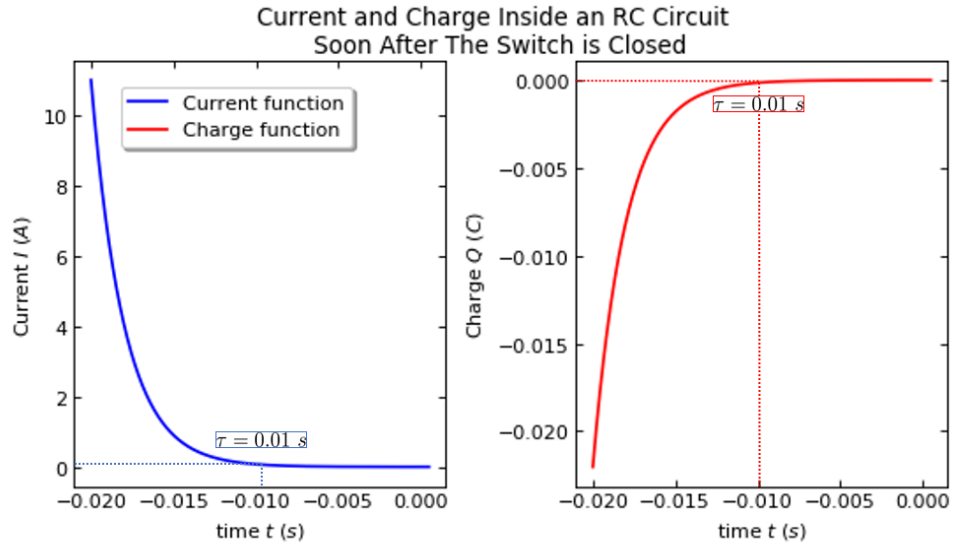


Figure 1: Current and Charge plots

Question 4.

a)

The inductor acts like a short therefore the steady current is

$$I = \frac{V_0}{R_1}.$$

b)

Since the switch is opened no current is going through R_1 such that,

$$\begin{aligned} \frac{dI}{dt} &= \frac{-R_2}{L} I \implies \frac{dI/dt}{I} = \frac{-R_2}{L} \\ \ln(I) &= \int \frac{-R_2}{L} dt = \frac{-R_2}{L} t + C. \\ \implies I(t) &= Ae^{\frac{-t}{\tau}} \quad \text{for } A = e^C. \end{aligned}$$

$$\text{Since } I(0) = \frac{V_0}{R_1} \implies I(t) = \frac{V_0}{R_1} e^{\frac{-t}{\tau}} \text{ , for } \tau = \frac{L}{R_2}.$$

c)

The total energy at time t formula is given by

$$U_L = \frac{1}{2} L (I(t))^2$$

Integrating from $0 \rightarrow t$ this formula whilst substituting the previous value found for $I(t)$,

$$\begin{aligned} U_L &= \frac{1}{2} L \left(\frac{V_0}{R_1} e^{\frac{-t}{\tau}} \right)^2 \\ &= \frac{V_0^2}{R_1^2} \frac{1}{2} L \int_0^t e^{\frac{-2t}{\tau}} dt \\ &= \frac{V_0^2}{R_1^2} \frac{1}{2} L (\tau (1 - e^{\frac{-2t}{\tau}})) \end{aligned}$$

$$\implies U_L = \frac{V_0^2}{R_1^2} \frac{1}{2} L (\tau (1 - e^{\frac{-2t}{\tau}}))$$

Taking the lim as $t \rightarrow \infty$ yields

$$\lim_{t \rightarrow \infty} U_L = \frac{V_0^2}{R_1^2} \frac{L\tau}{2}$$

Question 5.

Since potential difference is conserved in loops, we have

$$\begin{aligned} V_0 - IR_1 - L \frac{dI_1}{dt} &= V_0 - IR_1 - I_2 R_2 \\ \implies L \frac{dI_1}{dt} &= I_2 R_2. \end{aligned}$$

Three equations are necessary to solve this problem

1. $I = I_1 + I_2$ by the Mesh Law.
2. $L \frac{dI_1}{dt} = I_2 R_2$.

$$3. V_0 = R_1 I + L \frac{dI_1}{dt}$$

$$\begin{aligned} V_0 &= R_1 I + L \frac{dI_1}{dt} \\ &= R_1 I_1 + R_1 I_2 + L \frac{dI_1}{dt} \end{aligned}$$

Since $I_2 = \frac{L}{R_2} \frac{dI_1}{dt}$, we have

$$\begin{aligned} &= R_1 I_1 + \frac{R_1}{R_2} L \frac{dI_1}{dt} + L \frac{dI_1}{dt} \\ &= R_1 I_1 + \left(\frac{R_1}{R_2} + 1 \right) L \frac{dI_1}{dt} \\ \implies \frac{dI_1}{dt} &= \frac{V_0 - R_1 I_1}{L \left(1 + \frac{R_1}{R_2} \right)} \\ \frac{dI_1/dt}{V_0 - R_1 I_1} &= \frac{1}{L \left(1 + \frac{R_1}{R_2} \right)} \\ \ln |V_0 - R_1 I_1| &= -R_1 \left(\frac{t}{L \left(1 + \frac{R_1}{R_2} \right)} + C \right) \end{aligned}$$

Let $A = e^{-R_1 C}$, we then have

$$V_0 - R_1 I_1 = A e^{\frac{-R_1 t}{L(1+R_1/R_2)}}$$

Let $B = A / -R_1$, we then have

$$I_1(t) = B e^{\frac{-t R_1}{L(1+R_1/R_2)}} + \frac{V_0}{R_1}$$

Using the initial condition $I(0) = 0$ since initially no current goes through,

$$\begin{aligned} I_1(0) &= B e^{\frac{-\infty R_1}{L(1+R_1/R_2)}} + \frac{V_0}{R_1} = \frac{V_0}{R_1} \\ \implies I_1(t) &= \frac{V_0}{R_1} \left(1 + e^{\frac{-t R_1}{L(1+R_1/R_2)}} \right) = \frac{V_0}{R_1} \left(1 + e^{\frac{-t}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right)}} \right) \xrightarrow{t \rightarrow \infty} \frac{V_0}{R_1} \end{aligned}$$

Which indeed agrees with the long time limit from Question 4.